

Henry Daniels-Koch  
 Physics 3020 – Methods of Computational Physics  
 Prof. Baumgarte  
 22 September 2015  
 Homework Set 2

**3.1** This problem concerns an electrical circuit with  $n$  loops.

(a) Using Kirchoff's Laws we find  $n$  linearly independent equations that will determine the  $n$  currents  $I_i$ . Due to conservation of charge, the current going into a node must equal the current leaving a node. Therefore,

$$\begin{aligned} I_1 &= I_2 + I_3 + \dots + I_n \\ I_1 - I_2 - I_3 - \dots - I_n &= 0 \end{aligned} \tag{1}$$

Additionally, due to the conservation of energy, the voltage around a closed loop must be 0. We can write  $n - 1$  equations for  $n - 1$  loops:

$$\begin{aligned} I_2 R_2 + I_1 R_1 &= V_1 + V_2 \\ I_3 R_3 + I_1 R_1 &= V_1 + V_3 \\ &\vdots \\ I_n R_n + I_1 R_1 &= V_1 + V_n \end{aligned} \tag{2}$$

Together, (1) and (2) form  $n$  linearly independent equations.

(b) We can write these equations in matrix form:

$$Ax = b \tag{3}$$

We form an  $n$  by  $n$  matrix from these equations with equation (1) forming the first row of matrix  $A$  and the  $n - 1$  equations in (2) forming the rest of the matrix. The  $b$  vector in the equation is just the constants on the right sides of the equations. We can now solve for the vector  $x$  which contains the currents.

We now implement this process in the function "currentSolve()". The program prompts the user for their desired number of loops, allocates the  $A$  and  $b$  matrices, prompts the user for voltages and resistances, and fills the matrices. Using "LUdmp", we create an upper and lower matrix in order to solve large matrices. Implementing the method `alu.solve()`, we solve for  $x$  to obtain each current  $I_i$ .

(c) Using 3 loops, and setting  $V_1 = 2V$ ,  $V_2 = -4V$ ,  $V_3 = 3V$ ,  $R_1 = 3\Omega$ ,  $R_2 = 2\Omega$ ,  $R_3 = 1\Omega$ , our code determines currents

$$\begin{aligned} I_1 &= 0.727273 \\ I_2 &= -2.09091 \\ I_3 &= 2.81818 \end{aligned} \tag{4}$$

(d) For any  $n$  number of loops, we consider  $R_i = 1\Omega$ ,  $V_1 = 1V$ , and all other  $V_i = 0$ . We can solve for the current  $I_1$  analytically as a function of  $n$ . We use equation (2) to determine:

$$\begin{aligned} I_1 + I_2 &= 1 \\ I_1 + I_3 &= 1 \\ &\vdots \\ I_1 + I_n &= 1 \\ \implies I_n &= 1 - I_1 \end{aligned} \tag{5}$$

This implies that all currents other than  $I_1$  are equal.

$$I_2 = I_3 = \dots = I_n \quad (6)$$

Using equations (1) and (6) , we now determine:

$$I_1 = (n - 1)I_n \quad (7)$$

Using equations (5) and (7), we solve for  $I_1$

$$\begin{aligned} I_1 &= (n - 1)(1 - I_n) \\ I_1 &= \frac{n - 1}{n} \end{aligned} \quad (8)$$

This result matches my code's results when I test for values of  $n$  such as 100.

(e) We now consider the case  $V_i = 1V$  and  $R_i = i\Omega$ . When  $n = 100$ , we determine  $I_1 = 0.99$ . In order to make a plot of  $I_1$  as a function of  $n$ , we create a table of values by iterating over values of  $n$  from  $n = 1$  to  $n = 100$  and find  $I_1$ .